

3 (Sem-1) ELE

2017

ELECTRONICS
(General)

Full Marks : 60

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

1. Fill in the blanks :

1×7=7

- (a) A device which converts a.c. voltage into d.c. voltage is called a _____.
- (b) The _____ of rectification is defined as the ratio of the d.c. output power to the input a.c. power.
- (c) The process of adding impurities to a pure semiconductor is called _____.
- (d) The voltage where the current starts to increase rapidly is called the _____ voltage of the diode.
- (e) The resistance offered by a doped semiconductor is called the _____ resistance.

8A/338

(Turn Over)

(2)

- (f) The reverse saturation current is dependent on _____.
- (g) Reverse breakdown voltage for a diode is typically greater than _____ V.

2. Answer the following questions : $2 \times 4 = 8$

- (a) What is Q-point?
- (b) What is diffusion capacitance?
- (c) What is peak-inverse voltage?
- (d) What is breakdown voltage?

3. Answer any *three* of the following questions : $5 \times 3 = 15$

- (a) Explain the working principle of bridge rectifier with diagram.
- (b) Explain how current flows in a *p-n-p* transistor.
- (c) Draw the characteristic curve of an SCR and explain.
- (d) What are the advantages of negative feedback?
- (e) What are the characteristics of an ideal OP-AMP?

8A/338

(Continued)

(3)

4. Answer any *three* of the following questions : $10 \times 3 = 30$

- (a) Explain the formation of depletion layer in a *p-n* junction diode. Draw the *V-I* characteristic curve of a *p-n* junction diode and explain different parts of it. $5 + 5 = 10$

- (b) Describe the working of an *n-p-n* transistor. What is leakage current? A transistor has an emitter current of 8 mA and α of 0.99. What is the value of the collector current? $5 + 3 + 2 = 10$

- (c) Distinguish between FETs and BJTs. What is the difference between JFET and MOSFET? Give the construction of an *n*-channel MOSFET with diagram. $3 + 3 + 4 = 10$

- (d) Draw the block diagram of a feedback amplifier and derive an expression for the voltage gain with feedback. What type of feedback is used in oscillation and why? An amplifier has a voltage gain of -100. The feedback ratio is -0.04. Find the voltage gain with feedback. $5 + 3 + 2 = 10$

8A/338

(Turn Over)

(4)

(e) Show how OP-AMP can be used as non-inverting amplifier. Also deduce the relation between input and output voltages. For the circuit of inverting amplifier, $R_f = 100 \text{ k}\Omega$, $R_1 = 10 \text{ k}\Omega$ and $v_i = 1 \text{ V}$, calculate voltage gain and output voltage. What is CMRR?

5+3+2=10

(f) Write short notes on any *two* of the following :

5×2=10

(i) Varactor diode

(ii) Tunnel diode

(iii) Zener diode

(iv) Schottky diode
