

2016

ELECTRONICS

(Major)

Paper : 2.2

(**Electric Circuits**)

Full Marks : 60

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

Answer Question Nos. **1** and **2** which are compulsory
and **three** questions from Section—A, and
three from Section—B

1. (a) A network contains linear resistors and ideal voltage sources. If the values of all the resistors are doubled, then the voltage across each resistor is
 - (i) halved
 - (ii) doubled
 - (iii) increased by four times
 - (iv) not changed

- (b) If each branch of a delta network has resistance $\sqrt{3}R$, then each branch of the equivalent star network has resistance
- (i) $\frac{R}{\sqrt{3}}$ (ii) $3R$
- (iii) $3\sqrt{3}R$ (iv) $\frac{R}{3}$
- (c) The maximum power that can be transferred to the load R_L from the voltage source in Fig. 1

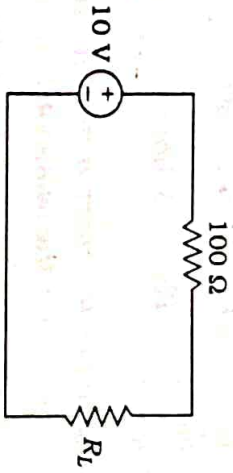


Fig. 1

- is
- (i) 1 W
- (ii) 10 W
- (iii) 0.25 W
- (iv) 0.5 W
- (d) Superposition theorem is not applicable to networks containing
- (i) non-linear elements
- (ii) dependant voltage source
- (iii) dependant current source
- (iv) transformers

A16/734

(Continued)

- (e) The average value of the current $i = 200 \sin t$ from $t = 0$ to $t = \pi/2$ is
- (i) 400π (ii) $400/\pi$
- (iii) $1/400$ (iv) $\pi/400$
- (f) A boiler at home is switched on to a.c. mains supplying power at 230 V, 50 Hz. The frequency of instantaneous power consumed is
- (i) 0 Hz
- (ii) 50 Hz
- (iii) 100 Hz
- (iv) 150 Hz
- (g) In a series R-L-C resonant circuit, the current is maximum at a frequency
- (i) equal to the resonant frequency
- (ii) greater than the resonant frequency
- (iii) less than the resonant frequency
- (iv) None of the above $1 \times 7 = 7$
2. (a) Two coupled coils with $L_1 = L_2 = 0.6$ H have a coupling coefficient of $K = 0.8$. What will be the turns ratio N_1 / N_2 ?
- (b) Four resistances 80 Ω, 50 Ω, 25 Ω and R are connected in parallel. Current through 25 Ω resistor is 4 A. Total current of the supply is 10 A. Then what is the value of R?

A16/734

(Turn Over)

- (c) Explain in short the basic principle of a potentiometer.
- (d) What is power in an a.c. circuit? Differentiate between active power and reactive power. 2×4=8

SECTION—A

Answer any three questions

- 3. Find the equivalent resistance between A and B in the network shown in Fig. 2. 5

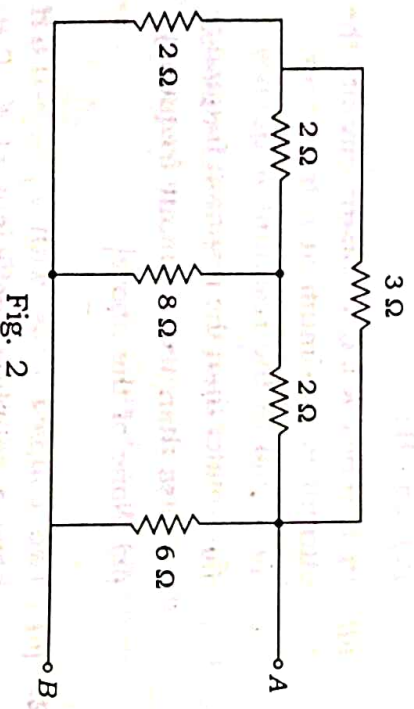


Fig. 2

- 4. From the defining equation for energy $W = \int_{-\infty}^t V(t)i(t) dt$ show that the energy stored by a capacitor is $W_C = \frac{1}{2} CV^2$ 5

- 5. Determine the current through the 5 Ω resistor of the network shown in Fig. 3 using mesh analysis : 5

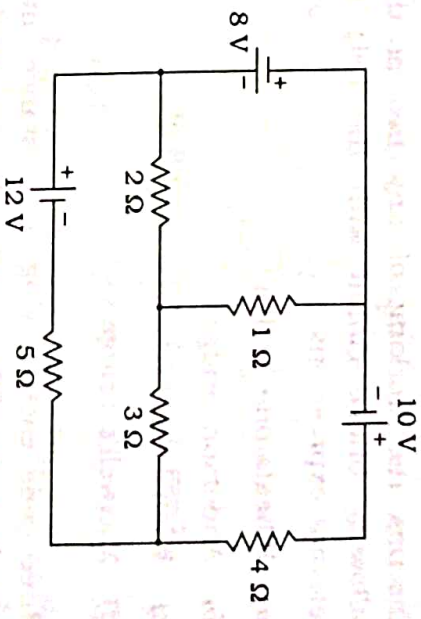


Fig. 3

- 6. Determine the current in the 5 Ω resistor of the network shown in Fig. 3 using superposition theorem. 5

- 7. Two impedances $z_1 = (20 + j10) \Omega$ and $z_2 = (10 - j30) \Omega$ are connected in parallel and this combination is connected in series with $z_3 = (30 + jX) \Omega$. Find the value of X which will produce resonance. 5

SECTION—B

Answer any three questions

8. Discuss the working of any two of the following bridge circuit with the help of relevant expressions : 5×2=10

- (a) Wheatstone bridge
- (b) Anderson bridge
- (c) Wien bridge
- (d) Maxwell's bridge

9. Three coils each having a resistance and an inductance of $8\ \Omega$ and $0.02\ \text{H}$ respectively, are connected in star across a 3-phase, 230 V, 50 Hz supply. Find the—

- (a) power factor;
- (b) line current;
- (c) power (real);
- (d) reactive volt-ampere;
- (e) total volt-ampere. 2×5=10

10. (a) Derive the relation for voltage, current and impedance of the primary side of an ideal transformer in terms of that of the secondary side and turns ratio. 6

- (b) State the Thevenin's theorem and explain with suitable example. 4

11. Find the voltage V_2 in the circuit shown in Fig. 4 such that current in the left-hand loop (loop-1) is zero. 10

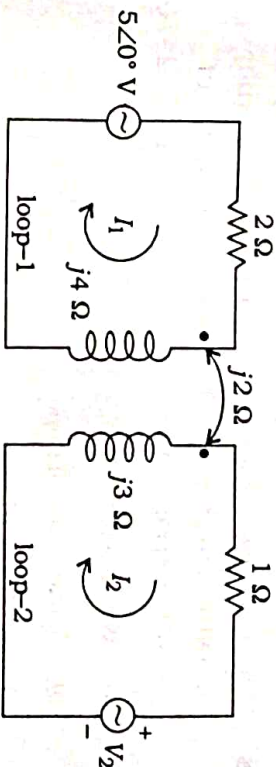


Fig. 4

12. A T-section low-pass filter has a series inductance of 60 mH having negligible resistance and a shunt element having a capacitance of $0.2\ \mu\text{F}$. Calculate—

- (a) cut-off frequency;
- (b) nominal impedance;
- (c) characteristic impedance at frequency 1 KHz and 5 KHz. 10

13. Write short notes on any two of the following : 5×2=10

- (a) Source transformation
- (b) Independent and controlled sources
- (c) Nodal analysis
- (d) Short-circuit test in transformer
- (e) Electromagnetism
