

Total number of printed pages-5

1 (Sem-3) ECT

**2024**

**ELECTRONICS AND COMMUNICATION  
TECHNOLOGY**

Paper : ECT0300104

**(Network Analysis)**

Full Marks : 45

Time : 2 hours

***The figures in the margin indicate  
full marks for the questions.***

1. Fill in the blanks : 1×5=5
- (a) A series network of resistors used for providing different voltages from a single voltage source is called \_\_\_\_\_ .
- (b) A filter allows a particular frequency range to pass which is known as \_\_\_\_\_ band.
- (c) The total resistance of a parallel circuit is always \_\_\_\_\_ than the lowest resistance connected in any of its branches.

Contd.

(d) A balanced form of  $\pi$ -section is also known as \_\_\_\_\_ section.

(e) If  $f(t) = 1$ , then  $F(s) =$  \_\_\_\_\_ .

2. Answer **any five** from the following questions : 2×5=10

(a) State Superposition Theorem.

(b) Define Ideal constant voltage source and Ideal constant current source.

(c) Draw a low-pass prototype filter (both T-section and  $\pi$ -section).

(d) Write the mathematical expression for Laplace Transform and Inverse Laplace Transform.

(e) In an RC-type low-pass filter,  $R = 550\Omega$  and  $f_c = 400\text{Hz}$ . Determine the value of C.

(f) What do you mean by Tree and Twigs in Network Theory?

(g) Define node and branch of a network.

(h) Determine the Laplace transform of an exponential function.

- (i) Draw the block diagram of a two-port network.
- (j) What are transfer Impedance and Admittance ?

3. Answer **any four** of the following questions :  
 $5 \times 4 = 20$

- (a) State and explain voltage division rule.
- (b) Transform the circuit from delta to Y:

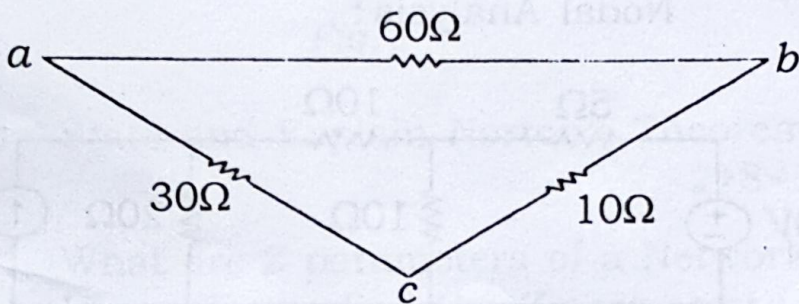


Fig. 1

- (c) What are poles and zeros in a network function ? Determine the poles and zeros of the transfer function given by

$$Z(s) = \frac{2(s+2)(s+4)}{(s+3)(s+5)(s+7)}$$

- (d) Derive the Step response of RL circuit using Laplace transform.

(e) Explain briefly the different types of graphs in network theory.

(f) Find the Laplace transform of a

derivative  $\left[ \frac{df(t)}{dt} \right]$ .

(g) Determine the current through  $20\Omega$  resistor in the following circuit using Nodal Analysis :

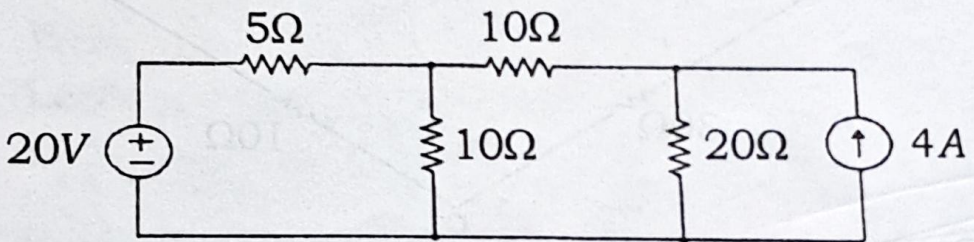


Fig. 2

(h) State and explain Reciprocity Theorem.

4. Answer **any one** of the following questions :

10

(a) What is Filter? Describe different types of Passive types of passive filters with proper diagrams.

2+8=10

- (b) State Thevenin's theorem. Apply Thevenin's theorem to find the current through load resistor  $R_L$  of the circuit given below. Here  $V_S = 20V$ ,  $R_1 = 10\Omega$ ,  $R_2 = 10\Omega$ ,  $R_3 = 5\Omega$  and  $R_L = 100\Omega$ . 2+8=10

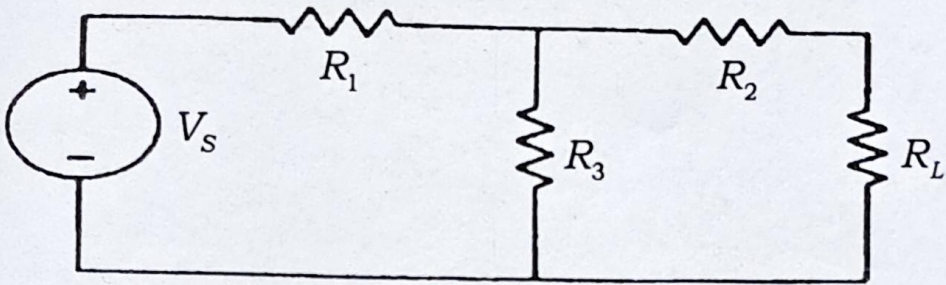


Fig. 3

- (c) State and Explain Norton's Theorem. 2+8=10
- (d) What are  $Z$  parameters of a Network? How will you find the  $Z$  parameters of the following two-port Network.

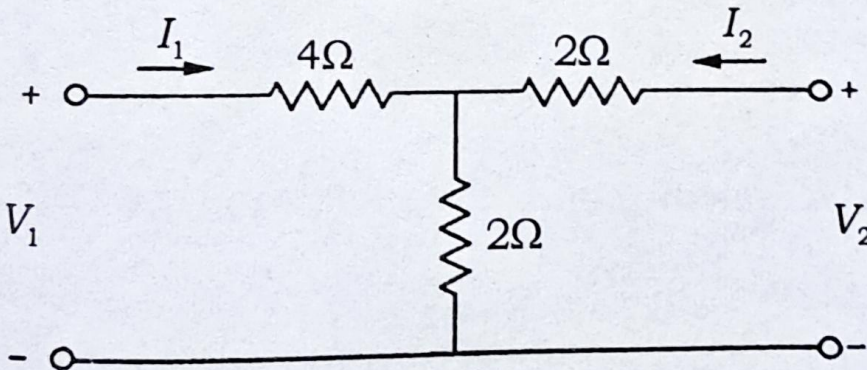


Fig. 4